

# Current and Resistance - Notes 5

Potential difference  $\hookrightarrow$  Voltage =  $\frac{\text{charge separation [PE]}}{\# \text{ charges in coulombs}} = \text{Volts} \quad V$


Current : the amt of nrg passing a point in a conductor  $\in$  second

: measured in amperes (A) by an ammeter

\* Conventional Current [backwards to the truth]

current flows from +  $\rightarrow$  -  $\star$  used to calculate Voltage and it's shown on circuit diagrams  
[but in reality  $e^- \rightarrow +$ ]

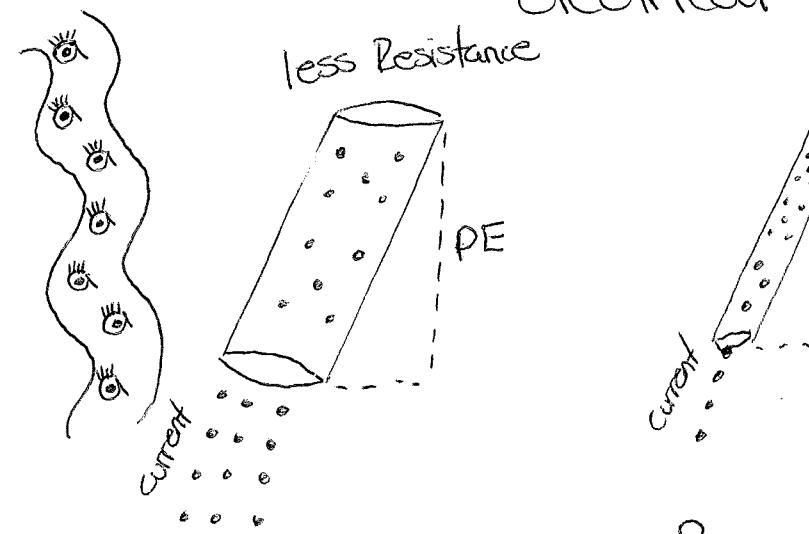Resistance: slows the flow of  $e^-$  and converts electrical nrg  $\rightarrow$  other nrg



Same PE  
Same charge  
 $\therefore$  Same Voltage

\* But less Resistance  
= greater current

More Resistance =  
Less current

R : resistance (ohms)

I : current (amps)

V : Voltage (volts)

$$R = \frac{V}{I}$$

$$V = IR$$