

# Ohm's Law - Notes 6

$$\text{Voltage} = \frac{PE}{\# \text{ of charges}}$$

[potential difference]

	What	Unit	Symbol
Voltage	volt(v)	V	
Current	ampere(A)	I	
Resistance	ohm ( $\Omega$ )	R	

## Ohm's Law

$$V = IR \quad \text{or} \quad \frac{V}{R} = I$$

or  $\frac{V}{I} = R$


Example: Current in circuit = 1.5A  
Potential difference = 12 V

What is the Resistance

$$R = \frac{V}{I} = \frac{12V}{1.5A} = 8 \Omega$$

Ex:

## Series Circuit H<sub>2</sub>O Slide

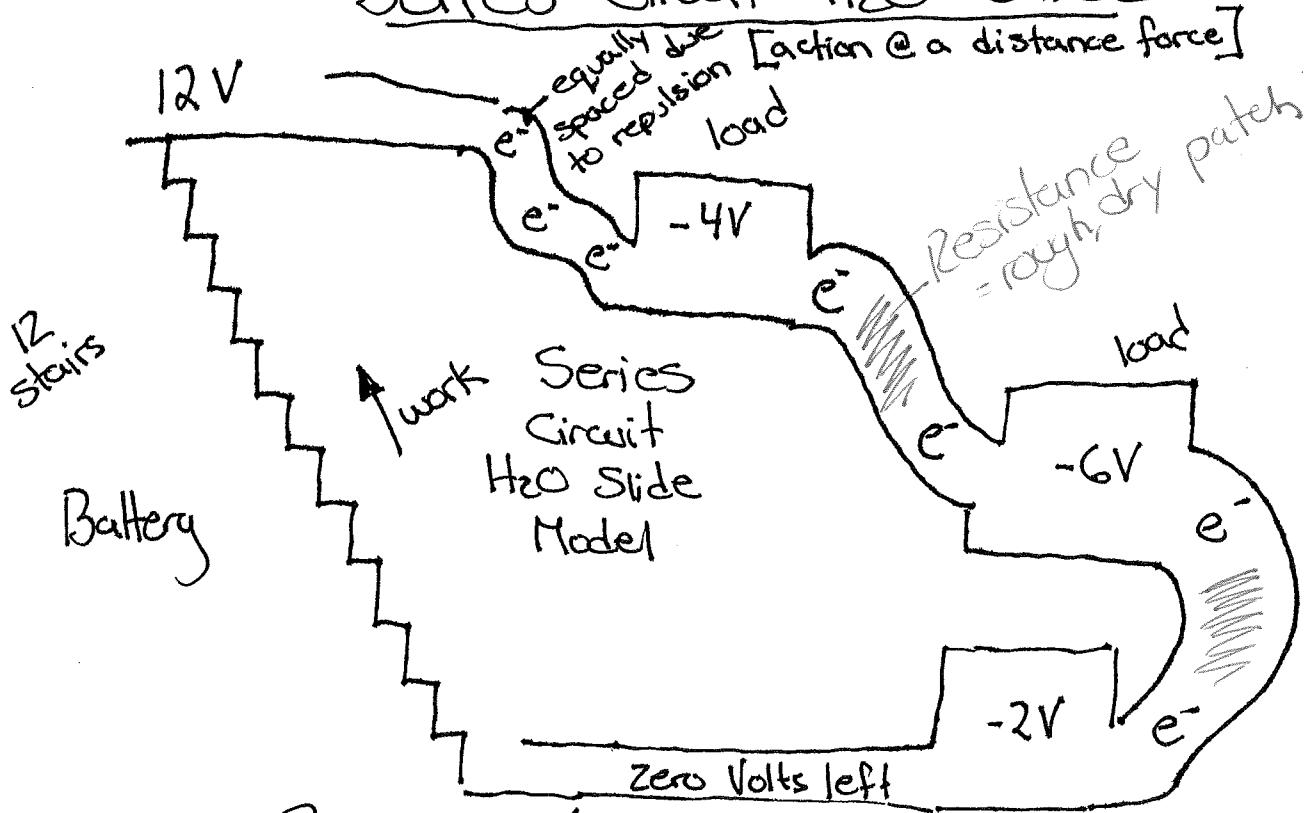

\*Series\*  
only 1 path for e- to flow

Resistance in Series  $\downarrow$  current

Current is constant in Series

Voltage  $\downarrow$  over the course of the circuit,  
as it is transformed by each load.